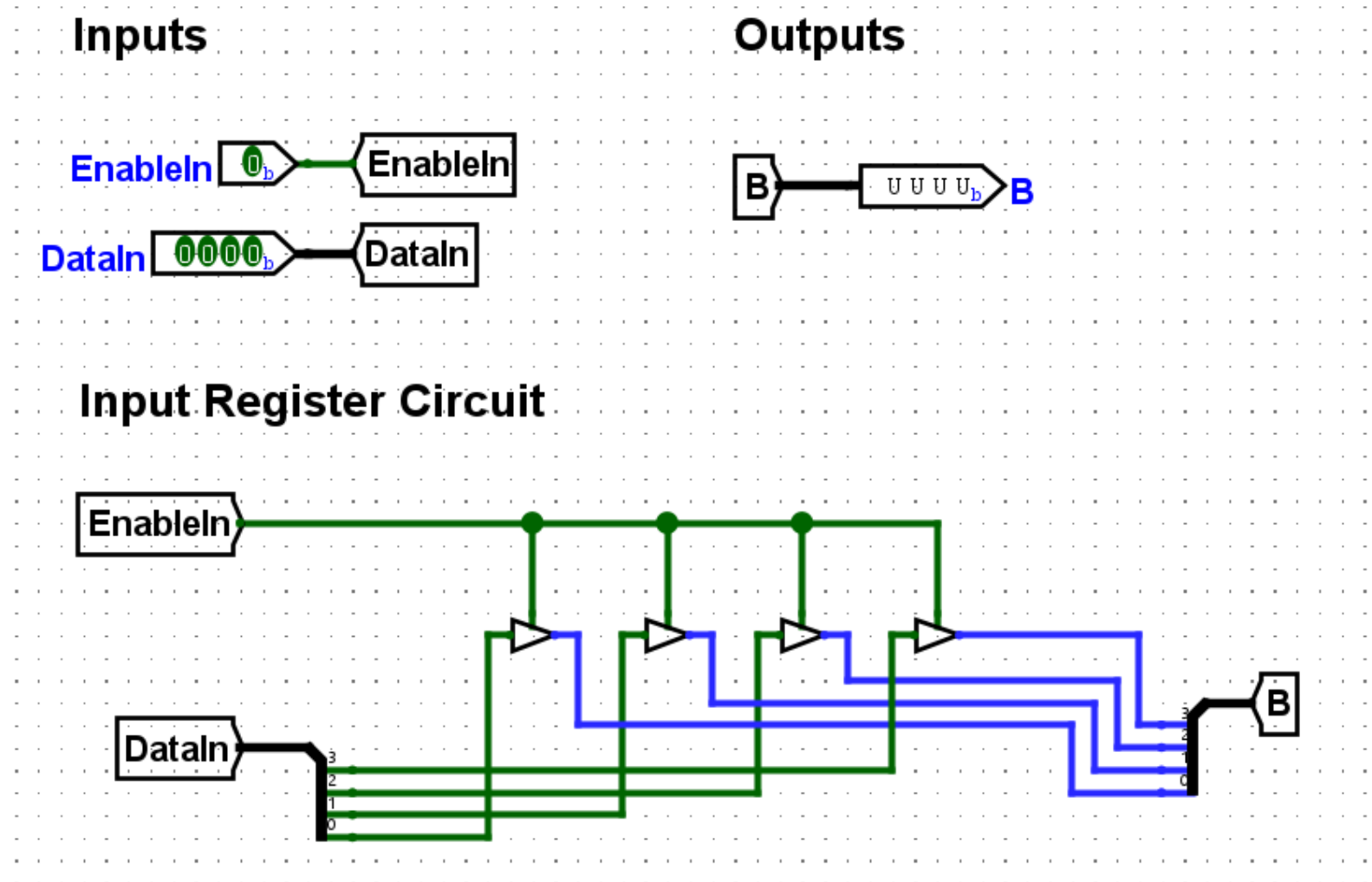



# In Register and Out Register for VSM

By: Rana Seif


# In Register




# Schematic

 

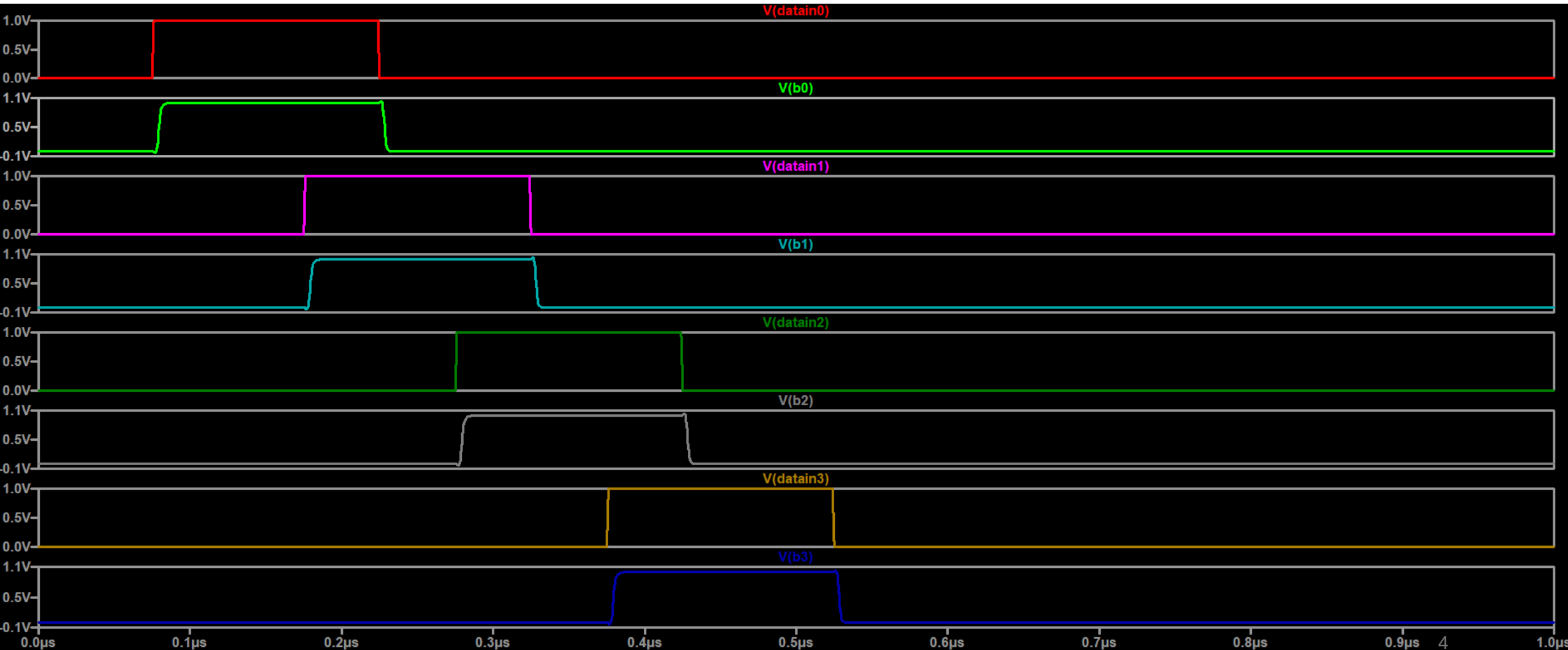
# Simulation Using SPICE (at EnableIn = 1)



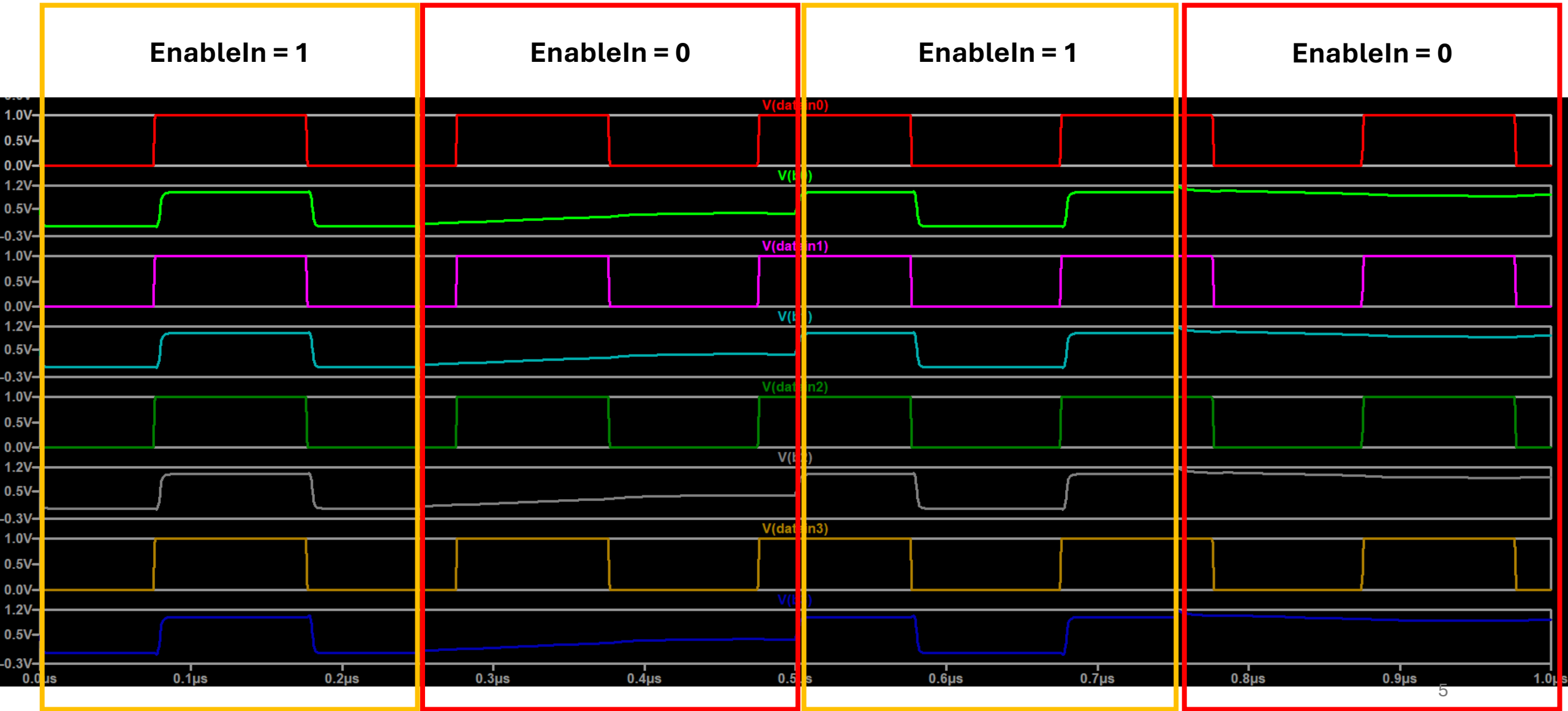
# Simulation Using SPICE (with Changing EnableIn)




EnableIn

 

# Out Register

 

# D Flip Flops From mudLib Library

 




# Schematic


A → Master Latch (on PH2)

B → Slave Latch (on PH1)


C → Logic in between latches  
(Also Source of Feedback)

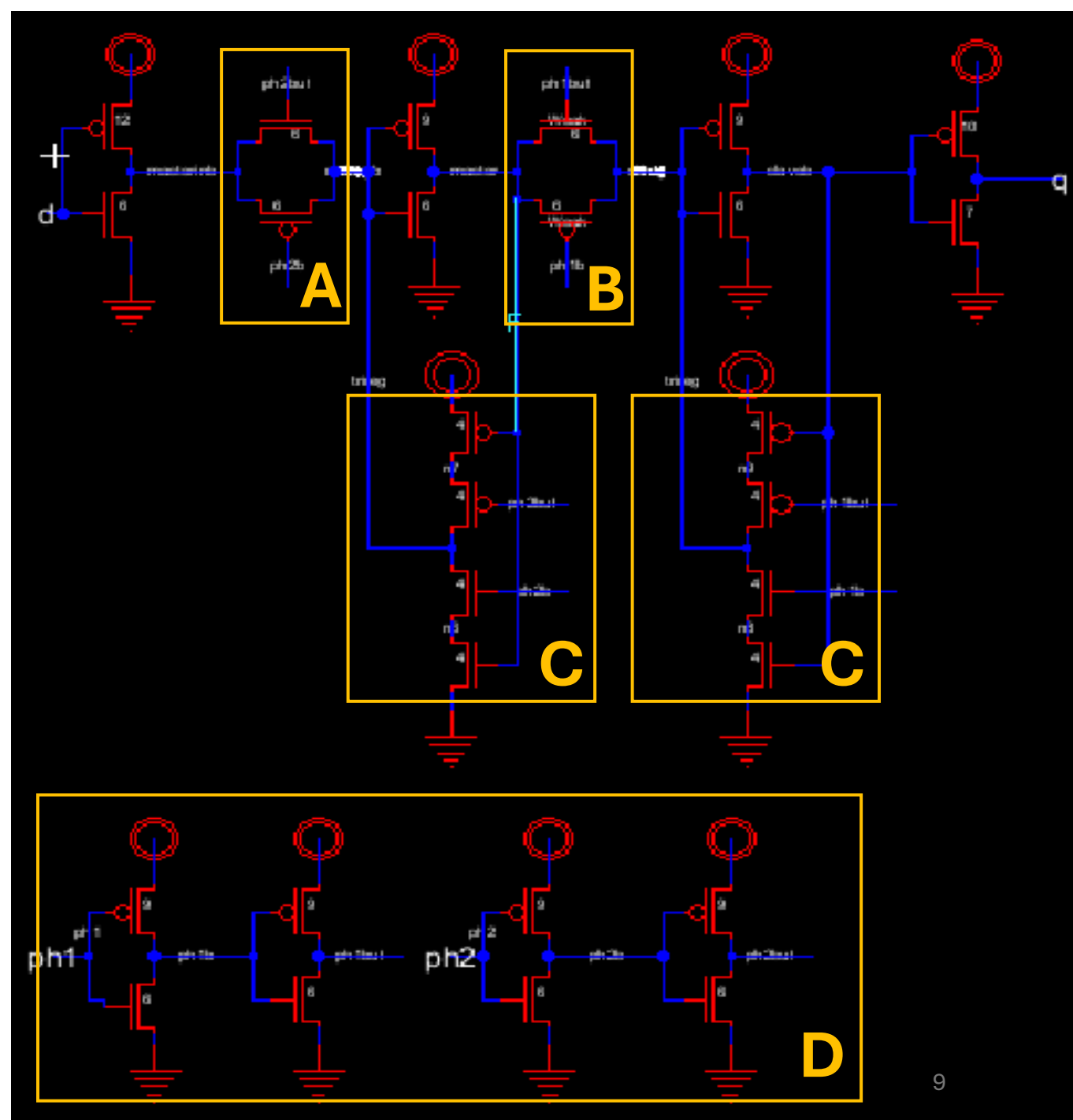D → Inverters to create inverted  
clocks and buffered clock signals



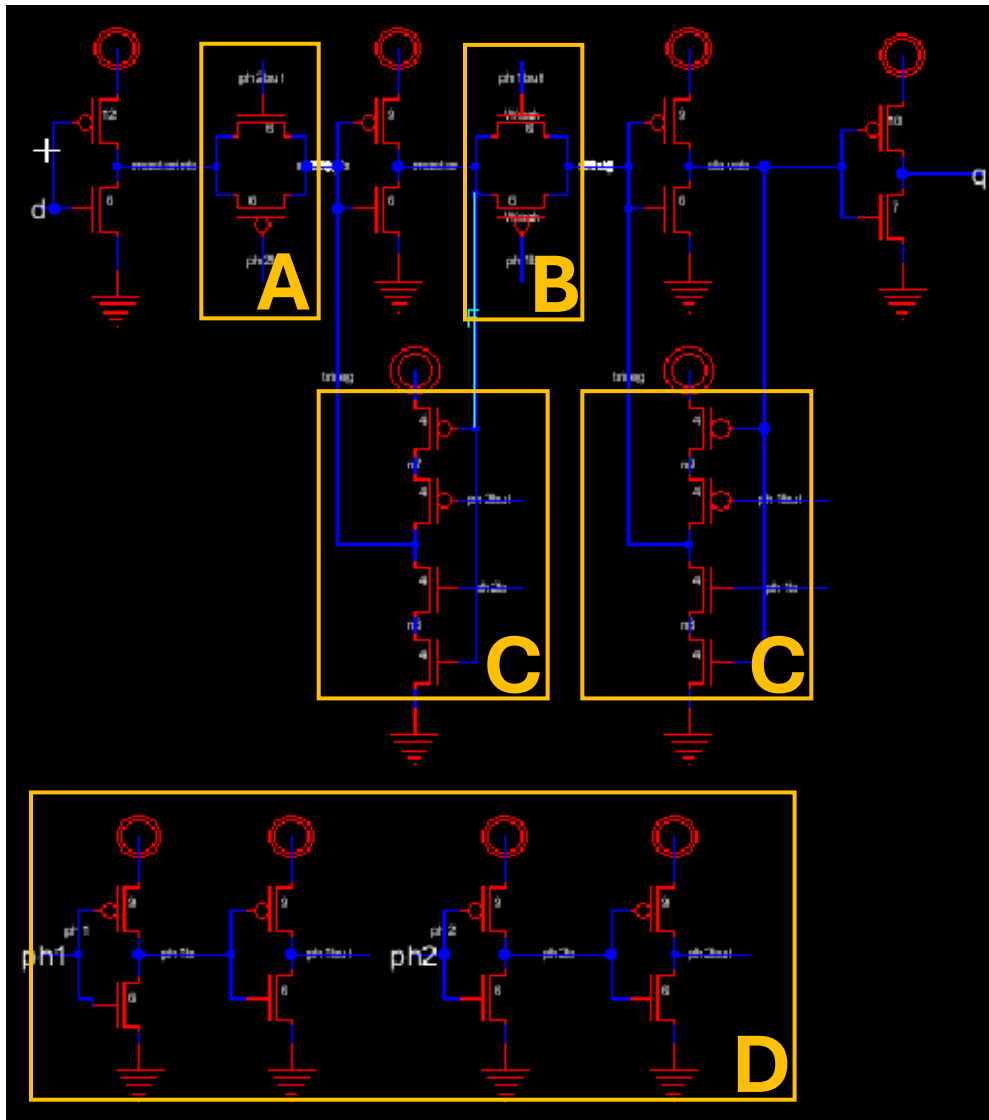

 
**Similarly behaving to D Flip-Flop with Master and Slave**




If we have overlapping clocks (including perfectly inverted), it triggered twice per clock cycle.

**So...** I decided to make my own D  
Flip-Flop

# D Flip-Flop

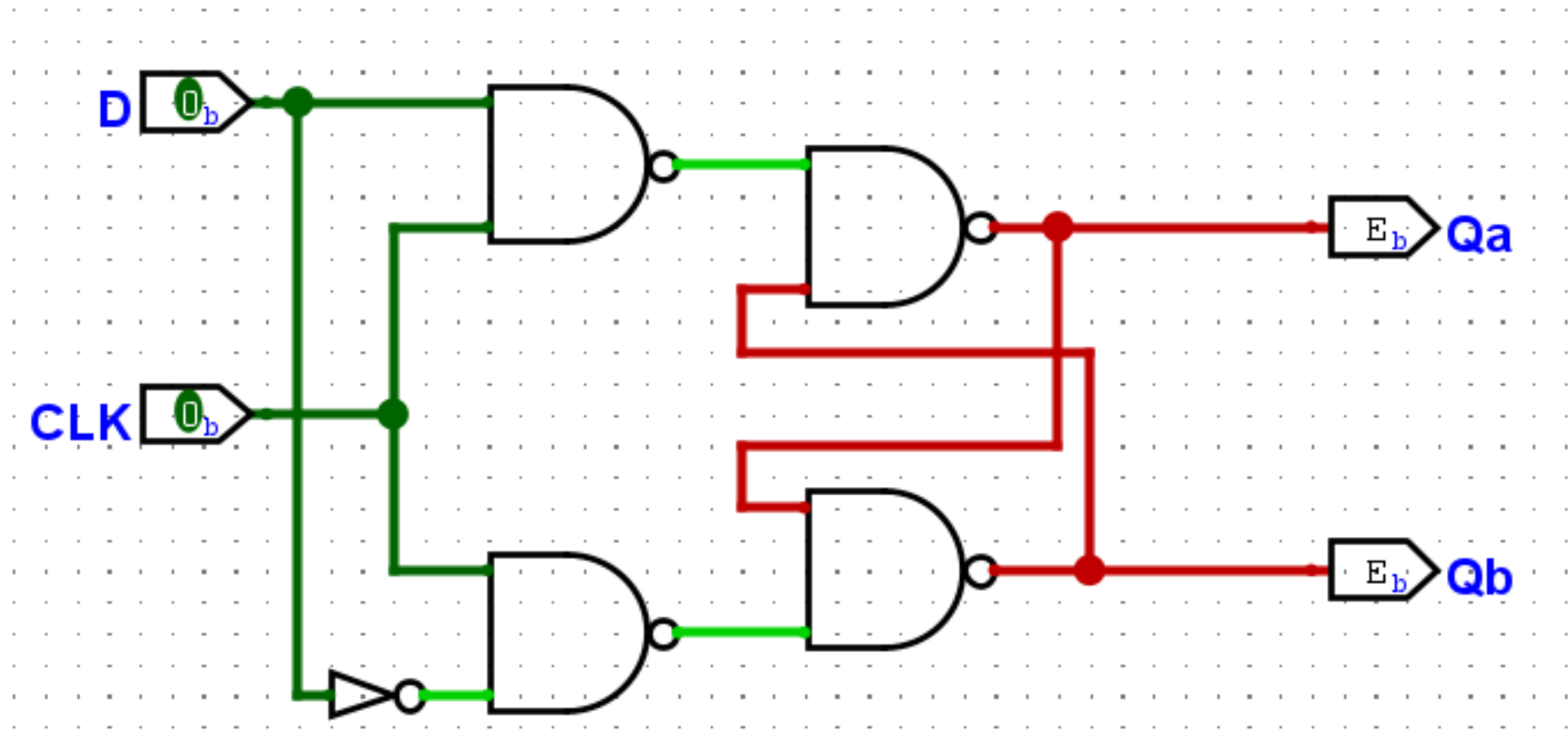


# Schematic

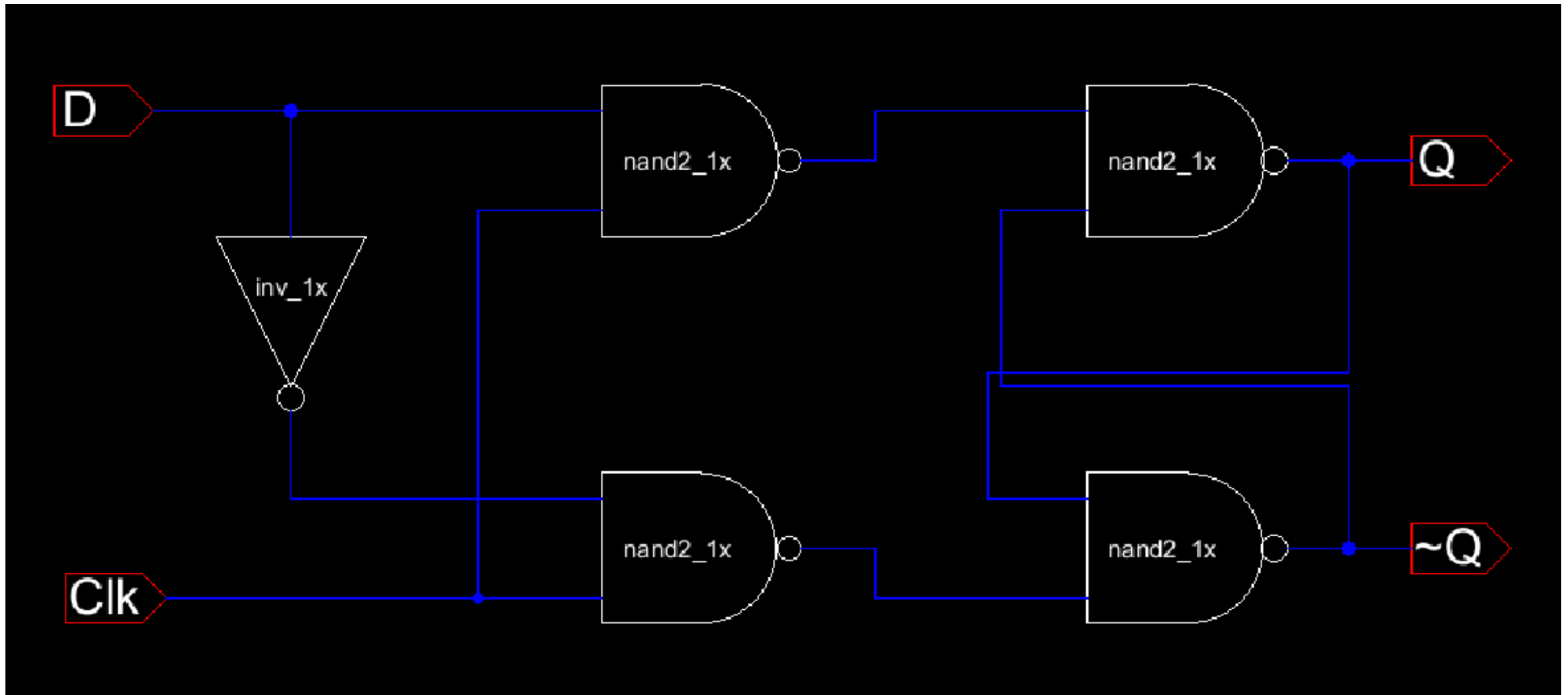


# Adding a Reset

In order to add a reset without fully redesigning the D Flip-Flop, we can use the following Truth Table

Reset	D	D_in
0	0	0
0	1	0
1	0	0
1	1	1

 


# Simulated Results of normal Flip-Flop

 


**Not Edge Triggered. Reflects D on output at all times when Clock is on**

# Edge Triggered D Flip-Flop


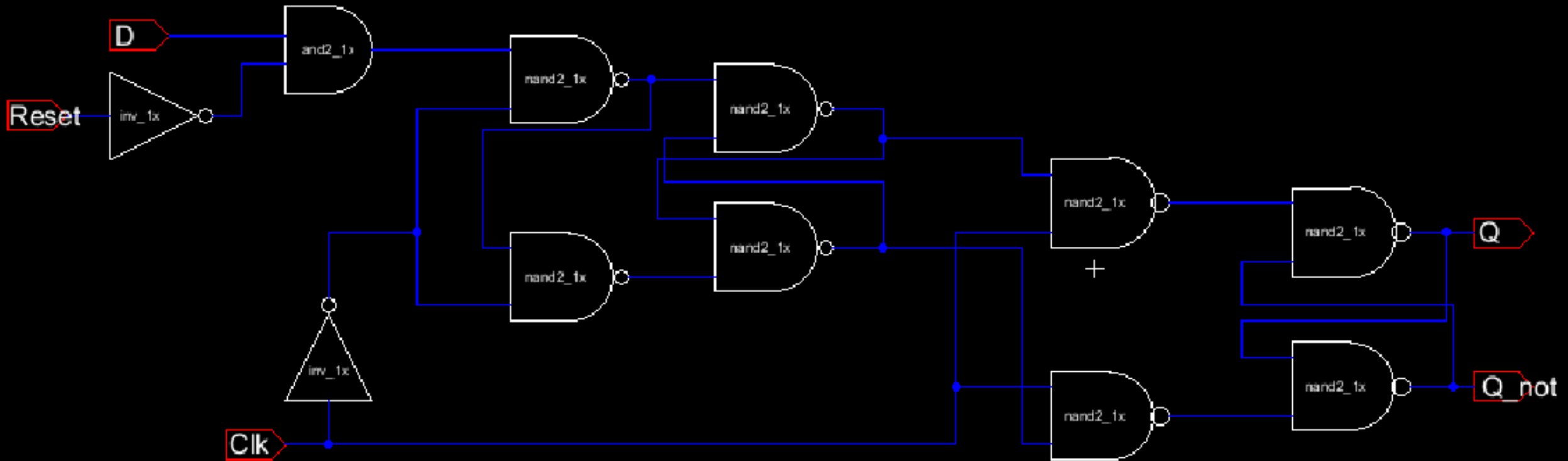





# Simulation Using SPICE

 


# Layout

  


# Back to Out Register

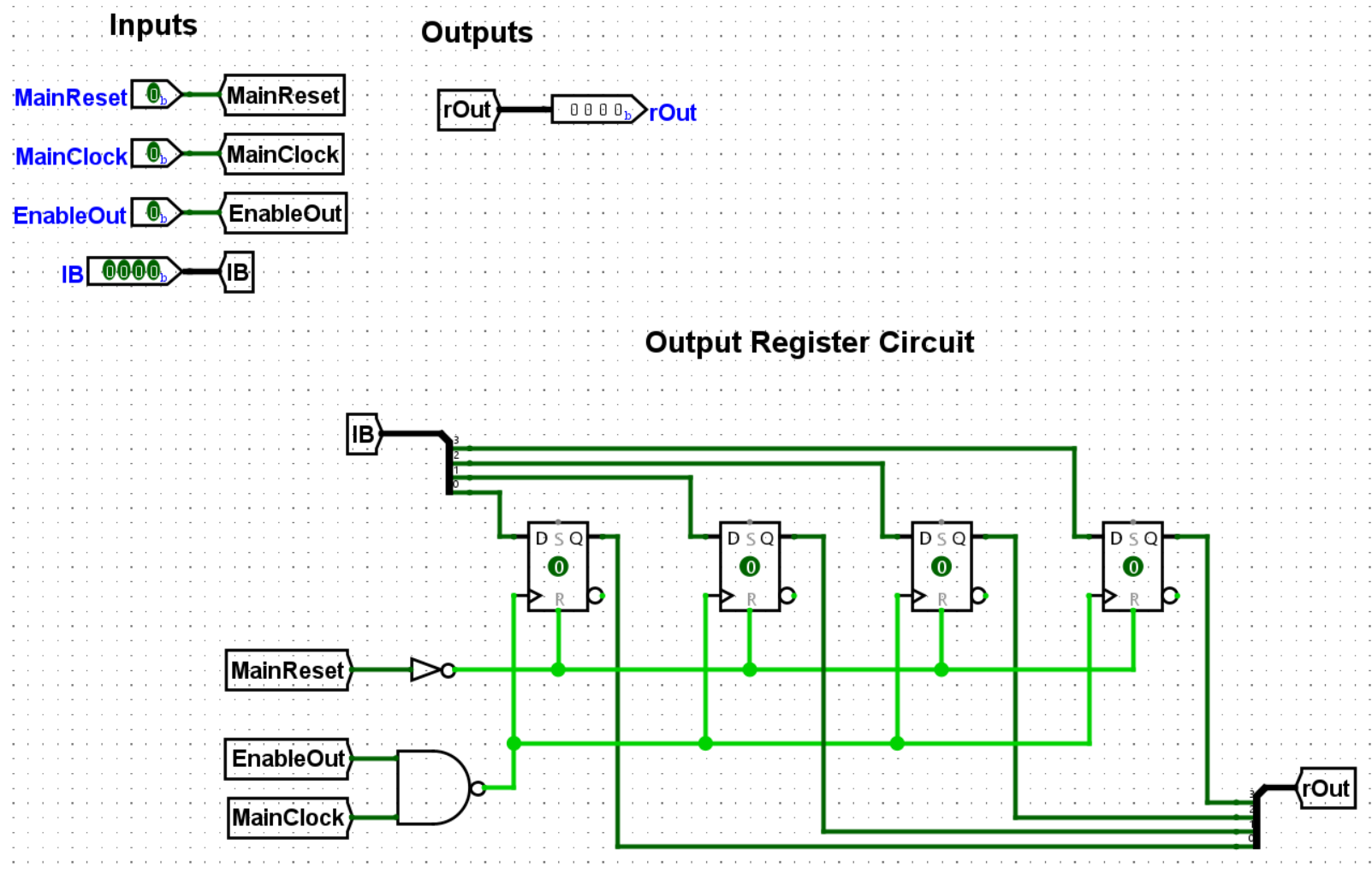



# Schematic

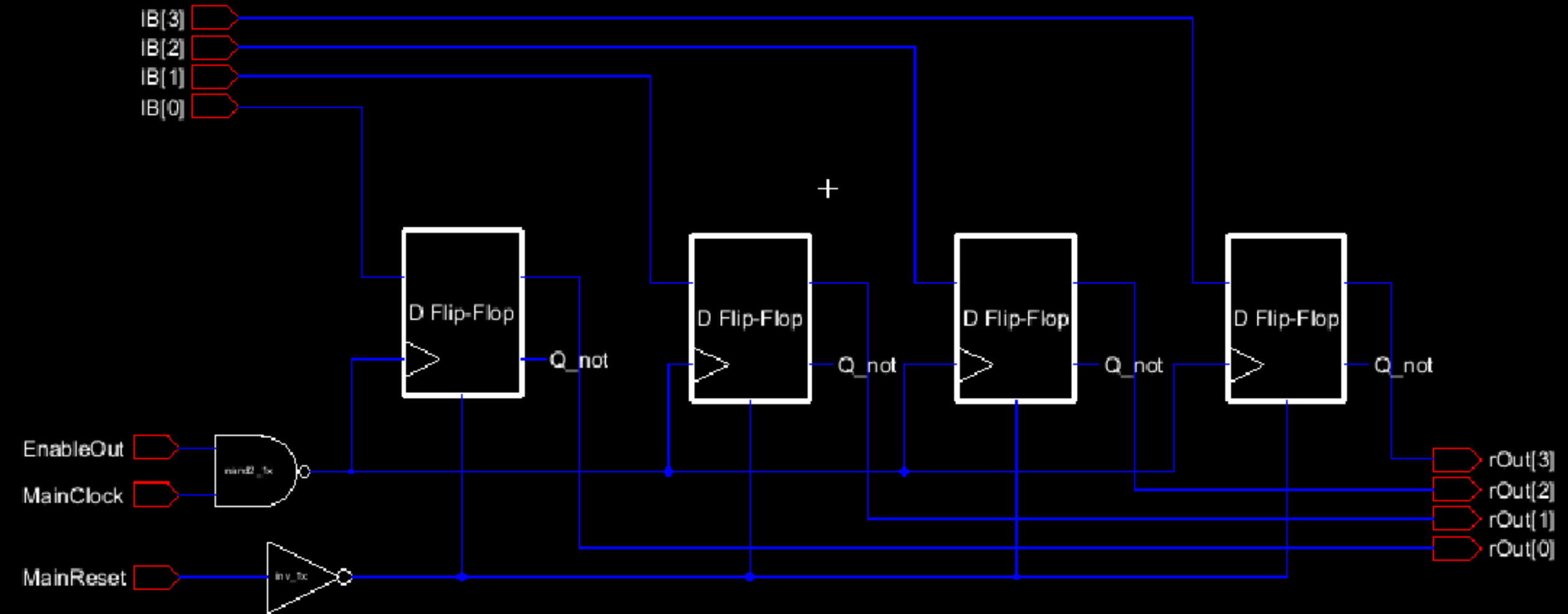
 
# Simulation Using SPICE (Enable and Reset = 1)



# Layout

  



THANK YOU FOR LISTENING